

**ISTANBUL TECHNICAL UNIVERSITY**  
**COMPUTER ENGINEERING DEPARTMENT**

**BLG 222E**  
**COMPUTER ORGANIZATION**  
**PROJECT 2 REPORT**

**CRN** : 21335

**LECTURER** : Deniz Turgay Altılar

**GROUP MEMBERS:**

150220022 : ALI EREN CIFTCI

150220033 : ISMAIL CIFTCI

**SPRING 2024**

# Contents

<b>1</b>	<b>INTRODUCTION</b>	<b>1</b>
<b>2</b>	<b>MATERIALS AND METHODS</b>	<b>1</b>
2.1	CPU System . . . . .	3
2.2	RTL Description . . . . .	4
2.2.1	ALL D . . . . .	4
2.2.2	D[0] D[1] D[2]: . . . . .	5
2.2.3	D[5] D[6]: . . . . .	5
2.2.4	D[7] D[8] D[9] D[10] D[11] D[14] D[24]: . . . . .	5
2.2.5	D[12] D[13] D[15] D[16] D[21] D[22] D[23] D[25] D[26] D[27] D[28] D[29]:	6
2.2.6	D[17] D[20]: . . . . .	8
2.2.7	D[18]: . . . . .	8
2.2.8	D[19]: . . . . .	8
2.2.9	D[30]: . . . . .	8
2.2.10	D[31]: . . . . .	8
2.2.11	D[32]: . . . . .	8
2.2.12	D[33]: . . . . .	8
2.3	Task Distribution . . . . .	9
<b>3</b>	<b>RESULTS</b>	<b>9</b>
3.1	Hardware . . . . .	9
3.2	Simulation . . . . .	11
<b>4</b>	<b>DISCUSSION</b>	<b>19</b>
<b>5</b>	<b>CONCLUSION</b>	<b>19</b>
	<b>REFERENCES</b>	<b>20</b>

# 1 INTRODUCTION

In this project a hardwired control unit was implemented and connected to the ALU System from the previous project. 33 operations were designed according to the given descriptions and then their control signals were implemented.

## 2 MATERIALS AND METHODS

The CPU system is comprised of an ALU system module from the previous project, and a hardwired control unit module. The instructions are stored in memory in little-endian order. Instructions are 16-bit long have two formats: with and without an address reference. 33 operations are described.

OPCODE (6-bit)	RSEL (2-bit)	ADDRESS (8-bit)
----------------	--------------	-----------------

Table 1: Instructions with an address reference.

OPCODE (6-bit)	S (1-bit)	DSTREG(3-bit)	SREG1 (3-bit)	SREG2 (3-bit)
----------------	-----------	---------------	---------------	---------------

Table 2: Instructions without an address reference.

The RSEL is a 2-bit field that specifies which Rx from RF is used. The S is a 1-bit field that specifies whether the flags will change or not The DSTREG is a 3-bit field that specifies the destination register. The SREG1 is a 3-bit field that specifies the first source register. The SREG2 is a 3-bit field that specifies the second source register.

RSEL	REGISTER
00	R1
01	R2
10	R3
11	R4

Table 3: RSEL table.

DSTREG/SREG1/SREG2	REGISTER
000	PC
001	PC
010	SP
011	AR
100	R1
101	R2
110	R3
111	R4

Table 4: DSTREG/SREG1/SREG2 selection table.

**OPCODE 0x00, BRA:**  $PC \leftarrow PC + \text{VALUE}$   
**OPCODE 0x01, BNE:** IF  $Z=0$  THEN  $PC \leftarrow PC + \text{VALUE}$   
**OPCODE 0x02, BEQ:** IF  $Z=1$  THEN  $PC \leftarrow PC + \text{VALUE}$   
**OPCODE 0x03, POP:**  $SP \leftarrow SP + 1$ ,  $R_x \leftarrow M[SP]$   
**OPCODE 0x04, PSH:**  $M[SP] \leftarrow R_x$ ,  $SP \leftarrow SP - 1$   
**OPCODE 0x05, INC:**  $\text{DSTREG} \leftarrow \text{SREG1} + 1$   
**OPCODE 0x06, DEC:**  $\text{DSTREG} \leftarrow \text{SREG1} - 1$   
**OPCODE 0x07, LSL:**  $\text{DSTREG} \leftarrow \text{LSL SREG1}$   
**OPCODE 0x08, LSR:**  $\text{DSTREG} \leftarrow \text{LSR SREG1}$   
**OPCODE 0x09, ASR:**  $\text{DSTREG} \leftarrow \text{ASR SREG1}$   
**OPCODE 0x0A, CSL:**  $\text{DSTREG} \leftarrow \text{CSL SREG1}$   
**OPCODE 0x0B, CSR:**  $\text{DSTREG} \leftarrow \text{CSR SREG1}$   
**OPCODE 0x0C, AND:**  $\text{DSTREG} \leftarrow \text{SREG1 AND SREG2}$   
**OPCODE 0x0D, ORR:**  $\text{DSTREG} \leftarrow \text{SREG1 OR SREG2}$   
**OPCODE 0x0E, NOT:**  $\text{DSTREG} \leftarrow \text{NOT SREG1}$   
**OPCODE 0x0F, XOR:**  $\text{DSTREG} \leftarrow \text{SREG1 XOR SREG2}$   
**OPCODE 0x10, NAND:**  $\text{DSTREG} \leftarrow \text{SREG1 NAND SREG2}$   
**OPCODE 0x11, MOVH:**  $R_x[15:8] \leftarrow \text{IMMEDIATE (8-bit)}$   
**OPCODE 0x12, LDR(16-bit):**  $R_x \leftarrow M[AR]$  (AR is 16-bit register)  
**OPCODE 0x13, STR(16-bit):**  $M[AR] \leftarrow R_x$  (AR is 16-bit register)  
**OPCODE 0x14, MOVL:**  $R_x[7:0] \leftarrow \text{IMMEDIATE (8-bit)}$   
**OPCODE 0x15, ADD:**  $\text{DSTREG} \leftarrow \text{SREG1} + \text{SREG2}$   
**OPCODE 0x16, ADC:**  $\text{DSTREG} \leftarrow \text{SREG1} + \text{SREG2} + \text{CARRY}$   
**OPCODE 0x17, SUB:**  $\text{DSTREG} \leftarrow \text{SREG1} - \text{SREG2}$

**OPCODE 0x18, MOVS:**  $\text{DSTREG} \leftarrow \text{SREG1}$ , Flags will change  
**OPCODE 0x19, ADDS:**  $\text{DSTREG} \leftarrow \text{SREG1} + \text{SREG2}$ , Flags will change  
**OPCODE 0x1A, SUBS:**  $\text{DSTREG} \leftarrow \text{SREG1} - \text{SREG2}$ , Flags will change  
**OPCODE 0x1B, ANDS:**  $\text{DSTREG} \leftarrow \text{SREG1} \text{ AND } \text{SREG2}$ , Flags will change  
**OPCODE 0x1C, ORRS:**  $\text{DSTREG} \leftarrow \text{SREG1} \text{ OR } \text{SREG2}$ , Flags will change  
**OPCODE 0x1D, XORS:**  $\text{DSTREG} \leftarrow \text{SREG1} \text{ XOR } \text{SREG2}$ , Flags will change  
**OPCODE 0x1E, BX:**  $\text{M}[\text{SP}] \leftarrow \text{PC}$ ,  $\text{PC} \leftarrow \text{Rx}$   
**OPCODE 0x1F, BL:**  $\text{PC} \leftarrow \text{M}[\text{SP}]$   
**OPCODE 0x20, LDRIM:**  $\text{Rx} \leftarrow \text{VALUE}$  (VALUE defined in ADDRESS bits)  
**OPCODE 0x21, STRIM:**  $\text{M}[\text{AR} + \text{OFFSET}] \leftarrow \text{Rx}$  (AR is 16-bit register) (OFFSET defined in ADDRESS bits)

## 2.1 CPU System

It has two inputs named Clock and Reset. Clock supplies the clock signal and Reset is used to give reset signal to the system. It has one 8-bit output named T that shows the sequence count the system is in. It contains an ArithmeticLogicUnitSystem module and a ControlUnit module. Outputs of the ControlUnit module is connected to the inputs of the ArithmeticLogicUnitSystem module.

**ControlUnit:** It has two inputs named Clock, Reset and a 16-bit input named IROut pulled from the ArithmeticLogicUnitSystem. It has outputs for the control signal inputs needed by ArithmeticLogicUnitSystem, as given in the following table.

CU Outputs	ALUS Inputs
RF_OutASel	RF_OutASel
RF_OutBSel	RF_OutBSel
RF_FunSel	RF_FunSel
RF_RegSel	RF_RegSel
ALU_WF	ALU_WF
ALU_FunSel	ALU_FunSel
ARF_OutCSel	ARF_OutCSel
ARF_OutDSel	ARF_OutDSel
ARF_FunSel	ARF_FunSel
ARF_RegSel	ARF_RegSel
IR_LH	IR_LH
IR_Write	IR_Write
Mem_WR	Mem_WR
Mem_CS	Mem_CS
MuxCSel	MuxCSel
MuxASel	MuxASel
MuxBSel	MuxBSel

Table 5: ControlUnit (CU) outputs connected to ArithmeticLogicUnitSystem (ALUS) inputs.

## 2.2 RTL Description

33 operations were designed in RTL according to the given descriptions and according to these designs their control signals were implemented. Using a decoder the opcodes were transformed into a 33 digit binary code named D. Using D and the decoded version of the sequence counter named T as control signals we can describe the operations in RTL.

### 2.2.1 ALL D

T[0]: IROut(0-7) <- M[PC], PC <- PC + 1

T[1]: IROut(8-15) <- M[PC], PC <- PC + 1

T[2]: D <- Decode[IROut(10-15)], S <- IROut(9)

### 2.2.2 D[0]|D[1]|D[2]:

T[2]&D[1]&Z: SC<-0

T[2]&D[2]&!Z: SC<-0

T[2]: S1<-IROut(0-7)

T[3]: S2<-PC

T[4]: PC<-S1+S2, S1<-0, S2<-0, SC<-0

### D[3]:

T[2]: Rx(0-7)<-M[SP], SP<-SP+1

T[3]: Rx(8-15)<-M[SP], SP<-SP+1, SC<-0

### D[4]:

T[2]: SP<-SP-1

T[3]: M[SP]<-Rx(0-7), SP<-SP-1

T[4]: M[SP]<-Rx(8-15), SC<-0

### 2.2.3 D[5]|D[6]:

T[2]: DSTREG<-SREG1

T[3]&D[5]: DSTREG<-DSTREG+1, SC<-0

T[3]&D[6]: DSTREG<-DSTREG-1, SC<-0

### 2.2.4 D[7]|D[8]|D[9]|D[10]|D[11]|D[14]|D[24]:

for D[7] OP: LSL

for D[8] OP: LSR

for D[9] OP: ASR

for D[10] OP: CSL

for D[11] OP: CSR

for D[14] OP: NOT

for D[24] OP: ID, ALU\_WF<-S

**SREG1 in RF**

T[2]: DSTREG<- OP SREG1, SC<-0

**SREG1 in ARF, DSTREG in ARF**

T[2]: S1<-SREG1

T[3]: DSTREG<- OP S1, S1<-0, SC<-0

**SREG1 in ARF, DSTREG in RF**

T[2]: S1<-SREG1

T[3]: DSTREG<- OP S1

T[3]: S1<-0, SC<-0

## **2.2.5 D[12]|D[13]|D[15]|D[16]|D[21]|D[22]|D[23]|D[25]|D[26]|D[27]|D[28]|D[29]:**

for D[12] OP: AND

for D[13] OP: OR

for D[15] OP: XOR

for D[16] OP: NAND

for D[21] OP: ADD

for D[22] OP: ADD with carry

for D[23] OP: SUB

for D[25] OP: ADD, ALU\_WF<-S

for D[26] OP: SUB, ALU\_WF<-S

for D[27] OP: AND, ALU\_WF<-S

for D[28] OP: OR, ALU\_WF<-S

for D[29] OP: XOR, ALU\_WF<-S

**SREG1 in ARF, SREG2 in ARF, DSTREG in ARF**

T[2]: S1<-SREG1



T[3]: S2<-SREG2

T[4]: DSTREG<- S1 OP S2, S1<-0, S2<-0, SC<-0

**SREG1 in ARF, SREG2 in ARF, DSTREG in RF**

T[2]: S1<-SREG1

T[3]: S2<-SREG2

T[4]: DSTREG<- S1 OP S2

T[5]: S1<-0, S2<-0, SC<-0

**SREG1 in ARF, SREG2 in RF, DSTREG in ARF**

T[2]: S1<-SREG1

T[3]: DSTREG<-S1 OP SREG2, S1<-0, SC<-0

**SREG1 in ARF, SREG2 in RF, DSTREG in RF**

T[2]: S1<-SREG1

T[3]: DSTREG<-S1 OP SREG2

T[4]: S1<-0, SC<-0

**SREG1 in RF, SREG2 in ARF, DSTREG in ARF**

T[2]: S2<-SREG2

T[3]: DSTREG<-SREG1 OP S2, S2<-0, SC<-0

**SREG1 in RF, SREG2 in ARF, DSTREG in RF**

T[2]: S2<-SREG2

T[3]: DSTREG<-SREG1 OP S2

T[4]: S2<-0, SC<-0

**SREG1 in RF, SREG2 in RF, DSTREG in ARF/RF**

T[2]: DSTREG<-SREG1 OP SREG2, SC<-0

### 2.2.6 D[17]|D[20]:

T[2]&D[17]: DSTREG(7-0)<-IR(0-7), SC<-0

T[2]&D[20]: DSTREG(15-8)<-IR(0-7), SC<-0

### 2.2.7 D[18]:

T[2]: Rx(0-7)<-M[AR], AR<-AR+1

T[3]: Rx(8-15)<-M[AR], SC<-0

### 2.2.8 D[19]:

T[2]: M[AR]<-Rx(0-7), AR<-AR+1

T[3]: M[AR]<-Rx(8-15) SC<-0

### 2.2.9 D[30]:

T[2]: S1<-PC

T[3]: M[SP]<-S1(0-7), SP<-SP-1

T[4]: M[SP]<-S1(8-15)

T[5]: PC<-Rx

### 2.2.10 D[31]:

T[2]: SP<-SP+1

T[3]: PC(0-7)<-M[SP], SP<-SP+1

T[4]: PC(8-15)<-M[SP], SC<-0

### 2.2.11 D[32]:

T[2]: Rx<-IR(0-7), SC<-0

### 2.2.12 D[33]:

T[2]: S1<-IR(0-7)

T[3]: S2<-AR

T[4]: AR<-S1+S2, S1<-0, S2<-0

T[5]: M[AR]<-Rx(0-7), AR<-AR+1

T[6]: M[AR]<-Rx(8-15), SC<-0

## 2.3 Task Distribution

We did not make a definite distribution of responsibilities at the beginning of the project however contributions from each member came out to be as follows: Code writing for modules, Ali Eren CIFTCI; Code refinement and fixing, Ali Eren CIFTCI and Ismail CIFTCI; Report writing, Ismail CIFTCI; Final checks, Ali Eren CIFTCI and Ismail CIFTCI.

# 3 RESULTS

## 3.1 Hardware

These were the hardware designs and some simulation excerpts that we acquired from our modules using Vivado.

 


Figure 1: Control Unit

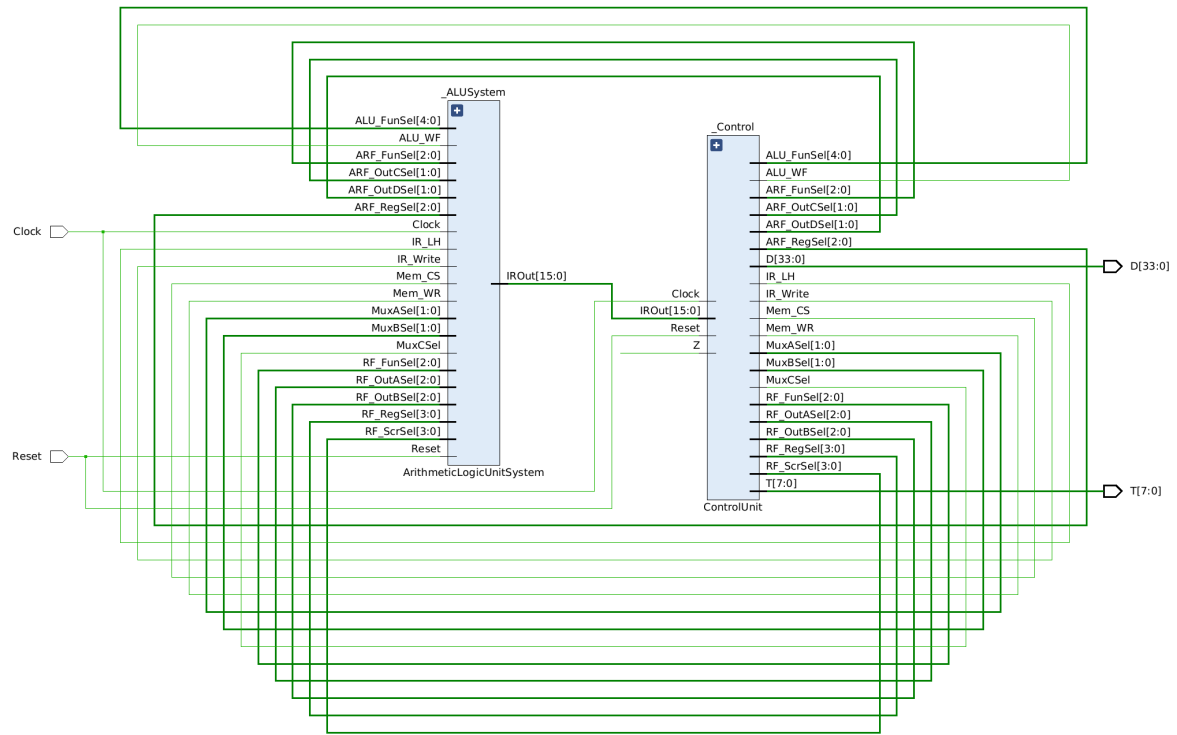


Figure 2: CPU System

## 3.2 Simulation

To test our code we wrote the given program in the following figure into our ram.mem file and the ran the simulation for 26300ns as this program needs this much time end.

1	28	//0028 BRA 0x28	(Branch to PC+40)
2	00		
3	00		
4	00		

Figure 3: Implemented program beginning.

41	00		
42	00		
43	00	//4400 MOVH R1 (branched to here)	
44	44		
45	0A	//500A MOVL R1	
46	50		
47	00	//4500 MOVH R2	
48	45		
49	00	//5100 MOVL R2	
50	51		
51	00	//4600 MOVH R3	
52	46		
53	B0	//52B0 MOVL R3	
54	52		
55	F0	//62F0 MOVS AR R3	
56	62		
57	00	//4A00 LDR R3	
58	4A		
59	6E	//556E ADD R2 R2 R3	
60	55		
61	D8	//14D8 INC AR AR	
62	14		
63	20	//1920 DEC R1 R1	
64	19		
65	20	//6320 MOVS R1 R1	
66	63		
67	F4	//04F4 BNE 0xF4 (-12 in decimal)	
68	04		
69	D8	//14D8 INC AR AR	
70	14		
71	00	//4D00 STR R2	
72	4D		
73	00		
74	00		

Figure 4: Implemented program continued (row count starts from 1).

Excerpts fromt the results of some operations from the program are in the following figures.

```

Output Values:
T: 1
Address Register File: PC: 0, AR: 0, SP: 255
Instruction Register : x
Register File Registers: R1: 0, R2: 0, R3: 0, R4: 0
Register File Scratch Registers: S1: 0, S2: 0, S3: 0, S4: 0
ALU Flags: Z: x, N: x, C: x, O: x
ALU Result: ALUOut: x
RAM_DATA[196] _ SONUC: 0

Output Values:
T: 2
Address Register File: PC: 1, AR: 0, SP: 255
Instruction Register : X
Register File Registers: R1: 0, R2: 0, R3: 0, R4: 0
Register File Scratch Registers: S1: 0, S2: 0, S3: 0, S4: 0
ALU Flags: Z: x, N: x, C: x, O: x
ALU Result: ALUOut: x
RAM_DATA[196] _ SONUC: 0

Output Values:
T: 4
Address Register File: PC: 2, AR: 0, SP: 255
Instruction Register : 40
Register File Registers: R1: 0, R2: 0, R3: 0, R4: 0
Register File Scratch Registers: S1: 0, S2: 0, S3: 0, S4: 0
ALU Flags: Z: x, N: x, C: x, O: x
ALU Result: ALUOut: 0
RAM_DATA[196] _ SONUC: 0

Output Values:
T: 8
Address Register File: PC: 2, AR: 0, SP: 255
Instruction Register : 40
Register File Registers: R1: 0, R2: 0, R3: 0, R4: 0
Register File Scratch Registers: S1: 40, S2: 0, S3: 0, S4: 0
ALU Flags: Z: x, N: x, C: x, O: x
ALU Result: ALUOut: 40
RAM_DATA[196] _ SONUC: 0

Output Values:
T: 16
Address Register File: PC: 2, AR: 0, SP: 255
Instruction Register : 40
Register File Registers: R1: 0, R2: 0, R3: 0, R4: 0
Register File Scratch Registers: S1: 40, S2: 2, S3: 0, S4: 0
ALU Flags: Z: x, N: x, C: x, O: x
ALU Result: ALUOut: 42
RAM_DATA[196] _ SONUC: 0

```

Figure 5: BRA 0x28

```

Output Values:
T: 1
Address Register File: PC: 56, AR: 176, SP: 255
Instruction Register : 25328
Register File Registers: R1: 10, R2: 0, R3: 176, R4: 0
Register File Scratch Registers: S1: 0, S2: 0, S3: 0, S4: 0
ALU Flags: Z: 0, N: 0, C: x, O: x
ALU Result: ALUOut: 0
RAM_DATA[196] _ SONUC: 0

Output Values:
T: 2
Address Register File: PC: 57, AR: 176, SP: 255
Instruction Register : 25088
Register File Registers: R1: 10, R2: 0, R3: 176, R4: 0
Register File Scratch Registers: S1: 0, S2: 0, S3: 0, S4: 0
ALU Flags: Z: 0, N: 0, C: x, O: x
ALU Result: ALUOut: 0
RAM_DATA[196] _ SONUC: 0

Output Values:
T: 4
Address Register File: PC: 58, AR: 176, SP: 255
Instruction Register : 18944
Register File Registers: R1: 10, R2: 0, R3: 176, R4: 0
Register File Scratch Registers: S1: 0, S2: 0, S3: 0, S4: 0
ALU Flags: Z: 0, N: 0, C: x, O: x
ALU Result: ALUOut: 0
RAM_DATA[196] _ SONUC: 0

Output Values:
T: 8
Address Register File: PC: 58, AR: 177, SP: 255
Instruction Register : 18944
Register File Registers: R1: 10, R2: 0, R3: 0, R4: 0
Register File Scratch Registers: S1: 0, S2: 0, S3: 0, S4: 0
ALU Flags: Z: 0, N: 0, C: x, O: x
ALU Result: ALUOut: 0
RAM_DATA[196] _ SONUC: 0

```

Figure 6: LDR R3

```

Output Values:
T: 1
Address Register File: PC: 58, AR: 177, SP: 255
Instruction Register : 18944
Register File Registers: R1: 10, R2: 0, R3: 0, R4: 0
Register File Scratch Registers: S1: 0, S2: 0, S3: 0, S4: 0
ALU Flags: Z: 0, N: 0, C: x, O: x
ALU Result: ALUOut: 0
RAM_DATA[196] _ SONUC: 0

Output Values:
T: 2
Address Register File: PC: 59, AR: 177, SP: 255
Instruction Register : 19054
Register File Registers: R1: 10, R2: 0, R3: 0, R4: 0
Register File Scratch Registers: S1: 0, S2: 0, S3: 0, S4: 0
ALU Flags: Z: 0, N: 0, C: x, O: x
ALU Result: ALUOut: 0
RAM_DATA[196] _ SONUC: 0

Output Values:
T: 4
Address Register File: PC: 60, AR: 177, SP: 255
Instruction Register : 21870
Register File Registers: R1: 10, R2: 0, R3: 0, R4: 0
Register File Scratch Registers: S1: 0, S2: 0, S3: 0, S4: 0
ALU Flags: Z: 0, N: 0, C: x, O: x
ALU Result: ALUOut: 0
RAM_DATA[196] _ SONUC: 0

```

Figure 7: ADD R2, R2, R3



```

Output Values:
T: 1
Address Register File: PC: 60, AR: 177, SP: 255
Instruction Register : 21870
Register File Registers: R1: 10, R2: 0, R3: 0, R4: 0
Register File Scratch Registers: S1: 0, S2: 0, S3: 0, S4: 0
ALU Flags: Z: 0, N: 0, C: x, O: x
ALU Result: ALUOut: 0
RAM_DATA[196] _ SONUC: 0

Output Values:
T: 2
Address Register File: PC: 61, AR: 177, SP: 255
Instruction Register : 21976
Register File Registers: R1: 10, R2: 0, R3: 0, R4: 0
Register File Scratch Registers: S1: 0, S2: 0, S3: 0, S4: 0
ALU Flags: Z: 0, N: 0, C: x, O: x
ALU Result: ALUOut: 0
RAM_DATA[196] _ SONUC: 0

Output Values:
T: 4
Address Register File: PC: 62, AR: 177, SP: 255
Instruction Register : 5336
Register File Registers: R1: 10, R2: 0, R3: 0, R4: 0
Register File Scratch Registers: S1: 0, S2: 0, S3: 0, S4: 0
ALU Flags: Z: 0, N: 0, C: x, O: x
ALU Result: ALUOut: 0
RAM_DATA[196] _ SONUC: 0

Output Values:
T: 8
Address Register File: PC: 62, AR: 177, SP: 255
Instruction Register : 5336
Register File Registers: R1: 10, R2: 0, R3: 0, R4: 0
Register File Scratch Registers: S1: 0, S2: 0, S3: 0, S4: 0
ALU Flags: Z: 0, N: 0, C: x, O: x
ALU Result: ALUOut: 0
RAM_DATA[196] _ SONUC: 0

```

Figure 8: INC AR, AR (first)

```

Output Values:
T: 1
Address Register File: PC: 66, AR: 178, SP: 255
Instruction Register : 25376
Register File Registers: R1: 9, R2: 0, R3: 0, R4: 0
Register File Scratch Registers: S1: 9, S2: 0, S3: 0, S4: 0
ALU Flags: Z: 0, N: 0, C: x, O: x
ALU Result: ALUOut: 9
RAM_DATA[196] _ SONUC: 0

Output Values:
T: 2
Address Register File: PC: 67, AR: 178, SP: 255
Instruction Register : 25588
Register File Registers: R1: 9, R2: 0, R3: 0, R4: 0
Register File Scratch Registers: S1: 9, S2: 0, S3: 0, S4: 0
ALU Flags: Z: 0, N: 0, C: x, O: x
ALU Result: ALUOut: 9
RAM_DATA[196] _ SONUC: 0

Output Values:
T: 4
Address Register File: PC: 68, AR: 178, SP: 255
Instruction Register : 1268
Register File Registers: R1: 9, R2: 0, R3: 0, R4: 0
Register File Scratch Registers: S1: 9, S2: 0, S3: 0, S4: 0
ALU Flags: Z: 0, N: 0, C: x, O: x
ALU Result: ALUOut: 9
RAM_DATA[196] _ SONUC: 0

Output Values:
T: 8
Address Register File: PC: 68, AR: 178, SP: 255
Instruction Register : 1268
Register File Registers: R1: 9, R2: 0, R3: 0, R4: 0
Register File Scratch Registers: S1: 65524, S2: 0, S3: 0, S4: 0
ALU Flags: Z: 0, N: 0, C: x, O: x
ALU Result: ALUOut: 65524
RAM_DATA[196] _ SONUC: 0

Output Values:
T: 16
Address Register File: PC: 68, AR: 178, SP: 255
Instruction Register : 1268
Register File Registers: R1: 9, R2: 0, R3: 0, R4: 0
Register File Scratch Registers: S1: 65524, S2: 68, S3: 0, S4: 0
ALU Flags: Z: 0, N: 0, C: x, O: x
ALU Result: ALUOut: 56
RAM_DATA[196] _ SONUC: 0

```

Figure 9: BNE 0xF4

```

Output Values:
T: 1
Address Register File: PC: 70, AR: 197, SP: 255
Instruction Register : 5336
Register File Registers: R1: 0, R2: 45, R3: 9, R4: 0
Register File Scratch Registers: S1: 0, S2: 0, S3: 0, S4: 0
ALU Flags: Z: 1, N: 0, C: x, O: x
ALU Result: ALUOut: 0
RAM_DATA[196] _ SONUC: 0

```

```

Output Values:
T: 2
Address Register File: PC: 71, AR: 197, SP: 255
Instruction Register : 5120
Register File Registers: R1: 0, R2: 45, R3: 9, R4: 0
Register File Scratch Registers: S1: 0, S2: 0, S3: 0, S4: 0
ALU Flags: Z: 1, N: 0, C: x, O: x
ALU Result: ALUOut: 0
RAM_DATA[196] _ SONUC: 0

```

```

Output Values:
T: 4
Address Register File: PC: 72, AR: 197, SP: 255
Instruction Register : 19712
Register File Registers: R1: 0, R2: 45, R3: 9, R4: 0
Register File Scratch Registers: S1: 0, S2: 0, S3: 0, S4: 0
ALU Flags: Z: 1, N: 0, C: x, O: x
ALU Result: ALUOut: 45
RAM_DATA[196] _ SONUC: 0

```

```

Output Values:
T: 8
Address Register File: PC: 72, AR: 196, SP: 255
Instruction Register : 19712
Register File Registers: R1: 0, R2: 45, R3: 9, R4: 0
Register File Scratch Registers: S1: 0, S2: 0, S3: 0, S4: 0
ALU Flags: Z: 1, N: 0, C: x, O: x
ALU Result: ALUOut: 45
RAM_DATA[196] _ SONUC: 45

```

Figure 10: STR R2

```

Output Values:
T: 1
Address Register File: PC: 72, AR: 196, SP: 255
Instruction Register : 19712
Register File Registers: R1: 0, R2: 45, R3: 9, R4: 0
Register File Scratch Registers: S1: 0, S2: 0, S3: 0, S4: 0
ALU Flags: Z: 1, N: 0, C: x, O: x
ALU Result: ALUOut: 0
RAM_DATA[196] _ SONUC: 45

```

Figure 11: END of program

194	00
195	09
196	00
197	00

Figure 12: This program is supposed to write the sum of values 0x1 to 0x9, which were contained within the cells from 0xB0 to 0xC3 (row count starts from 1), to the cells 0xC4 and 0xC5 in little endian form.

## 4 DISCUSSION

Using Verilog we described the control unit of the intended CPU in functional terms, connected it to the Arithmetic Logic Unit system and procured a design in Vivado using real-world hardware components such as wires, logic gates, buffers, latches, flip-flops, and multiplexers. Our system was simulated again in Vivado and the results were compared against given output examples and our understanding of the described system written in Verilog. We considered the results of these tests in correcting the designed system.

## 5 CONCLUSION

In this project the foremost difficulty we faced was in collecting the conditions for the control signals. For example if we had a mistake in one of our designs for an operation we would need to change a lot of components related to it. And because of the vastness of the code these changes were hard to keep track of. We acquired a better understanding of control signal hardwiring and a better understanding of RTL explanations of general operations.

## REFERENCES